



Ch.2 Boolean Algebra and Logic gates

Basic Definitions

- mathematical system 만족한다고 가정.
 - ① **Closure** : 자연수의 집합 내에서 닫혀 있음을 의미
 - ② **Associative law**(결합법칙)
 - ③ **Commutative law**(교환법칙)
 - ④ **Identity element**(항등원) : e 는 $*$ 연산자의 항등원, 0 은 $+$ 연산자의 항등원
 - ⑤ **Inverse**(역원)
 - ⑥ **Distributive law**(분배법칙)

Asiomatic Definition of Boolean Algebra

: Boolean 대수학적으로 정의 해보자면

Huntington의 가정

- closure ① [1-(a) Closure with respect to the operator +
1-(b) Closure with respect to the operator ·
- 항등원 ② [2-(a) An identity element with respect to the operator +, designed by 0:
 $0 + x = x + 0 = x$
2-(b) An identity element with respect to the operator ·, designed by 1:
 $1 \cdot x = x \cdot 1 = x$
- 교환 ③ [3-(a) commutative with respect to the operator +:
 $x + y = y + x$
3-(b) commutative with respect to the operator ·: $x \cdot y = y \cdot x$
- 분배 ④ [4-(a) · is distributive over +: $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$
4-(b) + is distributive over ·: $x + (y \cdot z) = (x + y) \cdot (x + z)$
- ⑤ 5. For every element $x \in B$, there exists an element $x' \in B$ $x' = \bar{x}$
(the complement of x) s.t. (a) $x + x' = 1$ and (b) $x \cdot x' = 0$
- ⑥ 6. There exists at least two elements $x, y \in B$ s.t. $x \neq y$

⇒ do not include the associative law → this law holds for Boolean Algebra

→ 공집합 문제도 되고 덧셈 문제도 가능!

- 4-(b) is valid for Boolean algebra, not for ordinary algebra
- Boolean algebra does not have additive or multiplicative inverse

Boolean vs. Ordinary algebra

- vs {
- Ordinary algebra : real number → infinite
 - Complement(보수) is not available in ordinary algebra.
 - Two-valued Boolean algebra : only two value {0,1}
 - Exactly same as the AND, OR(Binary), and NOT(Unary)
 - Huntington postulates are valid for {0,1}
 1. closure

$0+0=0$ $0+1=1+0=1$
 $1 \cdot 1 = 1$ $1 \cdot 0 = 0 \cdot 1 = 0$
 2. 진리표에 의해서 증명 가능
 3. The commutative law is obvious
 4. The distributive law holds true for two operator : from the truth tables

5. Form the complement table

6. is satisfied cuz only two values exist. $\rightarrow 0, 1$

Basic Theorems and Properties of Boolean Algebra

- **Duality(쌍대성)** : the dual of any equation which is true is always true

Postulates and Theorems of Boolean Algebra

Postulate 2	(a)	$x + 0 = x$	(b)	$x \cdot 1 = x$
Postulate 5	(a)	$x + x' = 1$	(b)	$x \cdot x' = 0$
Theorem 1	(a)	$x + x = x$	(b)	$x \cdot x = x$
Theorem 2	(a)	$x + 1 = 1$	(b)	$x \cdot 0 = 0$
Theorem 3, involution		$(x')' = x$		
Postulate 3, commutative	(a)	$x + y = y + x$	(b)	$xy = yx$
Theorem 4, associative	(a)	$x + (y + z) = (x + y) + z$	(b)	$x(yz) = (xy)z$
Postulate 4, distributive	(a)	$x(y + z) = xy + xz$	(b)	$x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a)	$(x + y)' = x'y'$	(b)	$(xy)' = x' + y'$
Theorem 6, absorption	(a)	$x + xy = x$	(b)	$x(x + y) = x$

Duality



\Rightarrow 진리표를 통해 증명도 가능

$$x(y+z) = xy + xz$$

$$x + yz = (x + y)(x + z)$$

- Some more laws

$$1. x + xy = x \rightarrow x(1+y) = x$$

$$2. xy + xy' = x \rightarrow x(y+y') = x$$

$$3. x + x'y = x + y \rightarrow (x+x')(x+y) = x+y$$

$$4. x(x+y) = x \rightarrow xx + xy = x + xy = x$$

$$5. (x+y)(x+y') = x \rightarrow x + (y+y') = x$$

$$6. x(x'+y) = xy \rightarrow xx' + xy = xy$$

$$7. xy + x'z + yz = xy + x'z$$

$$8. (x+y)(x'+z)(y+z) = (x+y)(x'+z)$$

$$8. (x+y)(z+x'y)$$

$$= xz + zy + x'y$$

$$= z(x+y) + x'y$$

$$= (x'+z)(x+y)$$

$$\rightarrow 7. xy + x'z + yz = xy + x'z + yz(x+x')$$

$$= xy + x'z + yzx + yzx'$$

$$= xy(1+z) + x'z(y+1)$$

$$= xy + x'z$$

Simplification of Boolean Function

$$\begin{aligned}
 F_2 &= x'y'z + x'yz + xy' \\
 &= x'z(y' + y) + xy' \\
 &= x'z + xy'
 \end{aligned}$$



등가

⇒ two different but equivalent circuits

⇒ Fewer gates is “better”

- cost less
- less power

⇒ fewer gate 찾기 위해 work 필요

 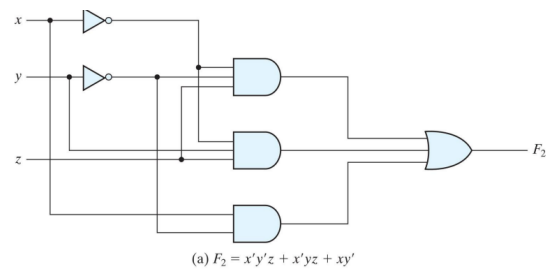

Algebraic Manipulation

- $x(x' + y) = xx' + xy = 0 + xy = xy$
- $x + x'y = (x + x')(x + y) = 1(x + y) = x + y$
- $(x + y)(x + y') = x + xy + xy' + yy' = x(1 + y + y') = x$
- $xy + x'z + yz = xy + x'z + yz(x + x')$
 $= xy + x'z + xyz + x'yz$
 $= xy(1 + z) + x'z(1 + y)$
 $= xy + x'z$
- $(x + y)(x' + z)(y + z) = (x + y)(x' + z)$, by duality from function 4

Complement of a Function

- $f(x, y, z) = x(y'z + yz)$
- De Morgan's law

$$\begin{aligned}
 f'(x, y, z) &= (x(y'z + yz))' \\
 &= x' + (y'z + yz)' \\
 &= x' + (y'z)'(yz)' \\
 &= x' + (y + z)(y' + z')
 \end{aligned}$$

[complement both sides]
 [because $(xy)' = x' + y'$]
 [because $(x + y)' = x' y'$]
 [because $(xy)' = x' + y'$, twice]

$\Rightarrow (x+y)' = x'y'$ (cuz the truth table)

x	y	$x + y$	$(x + y)'$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

x	y	x'	y'	$x'y'$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0

- dual of the func

If $f(x, y, z) = x(y'z' + yz)$

- The dual of f is $x + (y' + z')(y + z)$
- Then complementing each literal gives $x' + (y + z)(y' + z')$
- So, $f'(x, y, z) = x' + (y + z)(y' + z')$

$$f'(x, y, z) = x' (y'z' + yz)$$

- In general,

- $(A+B+C+ \dots + F)' = A'B'C' \dots F'$
- $(ABCD \dots F)' = A'+B'+C' \dots + F'$

Minterms

- a special product(AND) of literals (논리곱)
- n개의 variable \rightarrow 2의 n승 개의 minterms

Minterm	Is true when...	Shorthand
$x'y'z'$	$x = 0, y = 0, z = 0$	m_0
$x'y'z$	$x = 0, y = 0, z = 1$	m_1
$x'yz'$	$x = 0, y = 1, z = 0$	m_2
$x'yz$	$x = 0, y = 1, z = 1$	m_3
$xy'z'$	$x = 1, y = 0, z = 0$	m_4
$xy'z$	$x = 1, y = 0, z = 1$	m_5
xyz'	$x = 1, y = 1, z = 0$	m_6
xyz	$x = 1, y = 1, z = 1$	m_7

\rightarrow 순서 바뀌지 않음

• Sum of Minterms Form

- Every function can be written as a sum of minterms
- function output is 1 되는 minterm들의 합으로 function을 표현 가능

x	y	z	$f(x,y,z)$	$f'(x,y,z)$	
0	0	0	1	0	m_0
0	0	1	1	0	m_1
0	1	0	1	0	m_2
0	1	1	1	0	m_3
1	0	0	0	1	m_4
1	0	1	0	1	m_5
1	1	0	1	0	m_6
1	1	1	0	1	m_7

$f = x'y'z' + x'y'z + x'yz' + x'yz + xyz'$
 $= m_0 + m_1 + m_2 + m_3 + m_6$
 $= \Sigma(0,1,2,3,6)$

$f' = xy'z' + xy'z + xyz$
 $= m_4 + m_5 + m_7$
 $= \Sigma(4,5,7)$

f' contains all the minterms not in f


- dual idea($P \rightarrow S$, two level circuits)

- POS expression contains : only AND operations at the "outermost" lv.

ex. $f(x,y,z) = y'(x+y+z')(x+z)$

- POS expression can be implemented with two-level circuits

Lv1 : OR Gate
Lv2 : AND gate.

 

Maxterms (↔ Minterms)

- a sum of literals
- n개의 variable → 2의 n승 개의 maxterms

Maxterm	Is false when...	Shorthand
$x + y + z$	$x = 0, y = 0, z = 0$	M_0
$x + y + z'$	$x = 0, y = 0, z = 1$	M_1
$x + y' + z$	$x = 0, y = 1, z = 0$	M_2
$x + y' + z'$	$x = 0, y = 1, z = 1$	M_3
$x' + y + z$	$x = 1, y = 0, z = 0$	M_4
$x' + y + z'$	$x = 1, y = 0, z = 1$	M_5
$x' + y' + z$	$x = 1, y = 1, z = 0$	M_6
$x' + y' + z'$	$x = 1, y = 1, z = 1$	M_7

min

- **Product of maxterms form**

- Every function can be written as a unique product of maxterms.
- function output is 0 되는 maxterm들의 합으로 function을 표현 가능
minterm과 반대!!

x	y	z	$f(x,y,z)$	$f'(x,y,z)$
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1

$$\begin{aligned}
 f &= (x' + y + z)(x' + y + z')(x' + y' + z') \\
 &= M_4 M_5 M_7 \\
 &= \prod(4,5,7)
 \end{aligned}$$

$$\begin{aligned}
 f' &= (x + y + z)(x + y + z')(x + y' + z) \\
 &\quad (x + y' + z')(x' + y' + z) \\
 &= M_0 M_1 M_2 M_3 M_6 \\
 &= \prod(0,1,2,3,6)
 \end{aligned}$$

f' contains all the maxterms not in f

- **Minterms and maxterms are related**

- Any minterm m_i 은 maxterm M_i 의 complement

Minterms and Maxterms for Three Binary Variables

			Minterms		Maxterms	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

ex) $m_4' = M_4$

True

False



Converting between standard forms(POS , SOP)

$$f = \Sigma(0, 1, 2, 3, 6) \\ = \prod(4, 5, 7)$$

→ minterm에서 안 나온 number를 maxterm으로 converting

proof :

From before
and

complementing
so

$$f = \Sigma(0, 1, 2, 3, 6)$$

$$f' = \Sigma(4, 5, 7)$$

$$= m_4 + m_5 + m_7$$

$$(f')' = (m_4 + m_5 + m_7)'$$

$$f = m_4' m_5' m_7'$$

$$= M_4 M_5 M_7$$

$$= \prod(4, 5, 7)$$

[DeMorgan's law]

[By the previous page]

Standard forms of expressions


- 비용 적게 효율적으로 회로 제작 가능 (lv 단계의 수가 시간을 결정)
- 항상 Delay through gates.
- SOP expression contains
 - only OR operations at the "outermost" level.
 - using a two-level circuit 사용 (lv1. and + lv2. or)
 - NOT gates are implicit
 - literals are reused

- POS expression contains → duality

Standard Forms

⇒ 비용 ↓ 효율적으로 회로 제작 가능

lv. 단계가 시간 결정

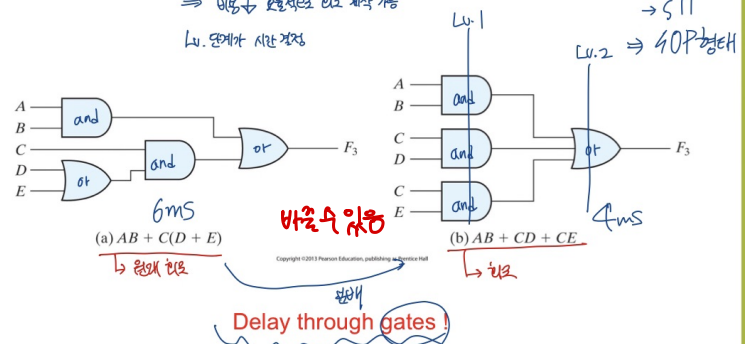

Other Logic Operations

Boolean Expressions for the 16 Functions of Two Variables









Boolean Functions	Operator Symbol	Name	Comments
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = xy'$	x/y	Inhibition	x , but not y
$F_3 = x$		Transfer	x
$F_4 = x'y$	y/x	Inhibition	y , but not x
$F_5 = y$		Transfer	y
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y , but not both
$F_7 = x + y$	$x + y$	OR	x or y
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	x equals y
$F_{10} = y'$	y'	Complement	Not y
$F_{11} = x + y'$	$x \supset y$	Implication	If y , then x
$F_{12} = x'$	x'	Complement	Not x
$F_{13} = x' + y$	$x \supset y$	Implication	If x , then y
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1

Truth Tables for the 16 Functions of Two Binary Variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Digital Logic Gate


Digital Logic Gate

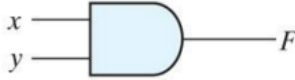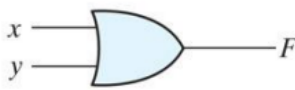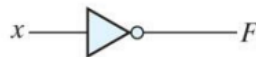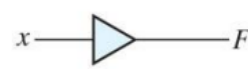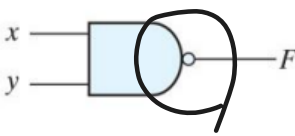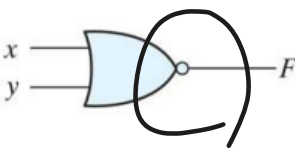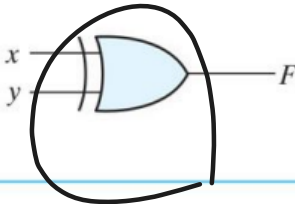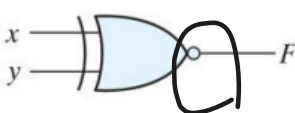Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = x \cdot y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	
① NAND	② 	③ $F = (xy)'$	④ <table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y$ $= x \oplus y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$F = xy + x'y'$ $= (x \oplus y)'$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

다르면 1


같은 1

 XOR gates \Rightarrow using 2 input gates



(a) Using 2-input gates

\hookrightarrow 일반적으로는 2-input 사용

 

(b) 3-input gate

\Rightarrow 짝수이면 0, 홀수이면 1


positive and negative logic

- positive logic


- low = 0, high = 1

- negative logic

- low = 1, high = 0

 

(a) Positive logic

 

(b) Negative logic

\Rightarrow positive logic의 사용.

Integrated Circuits(IC)

: 집적회로 \rightarrow 어떻게 분류?

Integrated Circuits (IC) 집적 회로

- Levels \rightarrow 한 칩에 들어 있는 chip(gate)의 수
 - SSI 10개 내의 chip
 - MSI: 10~1,000 gates 1000개 내의
 - LSI: thousands of gates 몇천개
 - VLSI: hundreds thousands of gates 수만개
- Digital Logic Families \rightarrow 소자 (용량) 에 따라서 나뉨.
 - TTL: transistor-transistor logic
 - ECL: emitter-coupled logic
 - MOS: Metal-oxide semiconductor
 - CMOS: Complementary metal-oxide semiconductor
- References
 - Fan-out \rightarrow 몇개의 회로를 부하할수 있느냐 (out) $\frac{1mA}{0.4mA/K}$ \hookrightarrow 전류를 다룰수 많음.
 - Fan-in " (in)
 - Power dissipation 전압 소비량
 - Propagation delay performance의 정도 \rightarrow 가변 결정 요인
 - Noise margin